

Voltage Drop

Contrary to common belief, the NEC generally doesn't require you to size conductors to accommodate voltage drop. It merely suggests in the Fine Print Notes to 210.19(A), 215.2(A)(4), 230.31(C), and 310.15(A)(1) that you adjust for voltage drop when sizing conductors. It's important for you to remember that Fine Print Notes are recommendations, not requirements [90.5(C)].

The NEC recommends that the maximum combined voltage drop for both the feeder and branch circuit shouldn't exceed 5%, and the maximum on the feeder or branch circuit shouldn't exceed 3% (**Fig. 1**). This recommendation is a performance issue, not a safety issue.

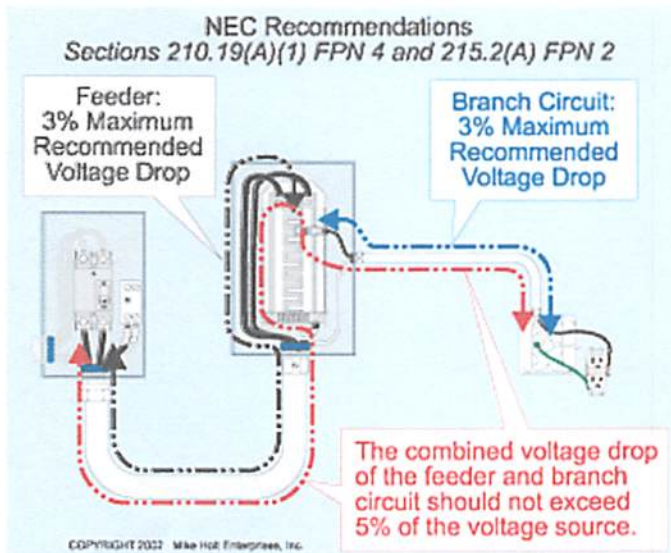


Fig. 1. These recommended voltage drops are performance-related.

If the NEC doesn't require you to size for voltage drop, why even think about it? Consider these reasons:

- *System efficiency.* If a circuit supports much of a load, a larger conductor will pay for itself many times over in energy savings alone.
- *System performance* Lighting loads perform best when voltage drop is minimal. You get the light of a higher-wattage system simply by running larger wires.
- *Troubleshooting* If you follow the NEC voltage drop recommendations, you don't have to guess whether your field measurements indicate a problem or if the voltage is low due to not accommodating voltage drop in the design.
- *Load protection* Undervoltage for inductive loads can cause overheating, inefficiency, and shorter life span of equipment. When conductor resistance causes the voltage to drop below an acceptable point, increase the conductor size.

What exactly is voltage drop? The voltage drop of a circuit is in direct proportion to the resistance of the conductor and the magnitude of the current. If you increase the length of a conductor, you increase its resistance — and thus increase its voltage drop. If you increase the

current, you increase the conductor voltage drop. Thus, long runs often produce voltage drops that exceed NEC recommendations.

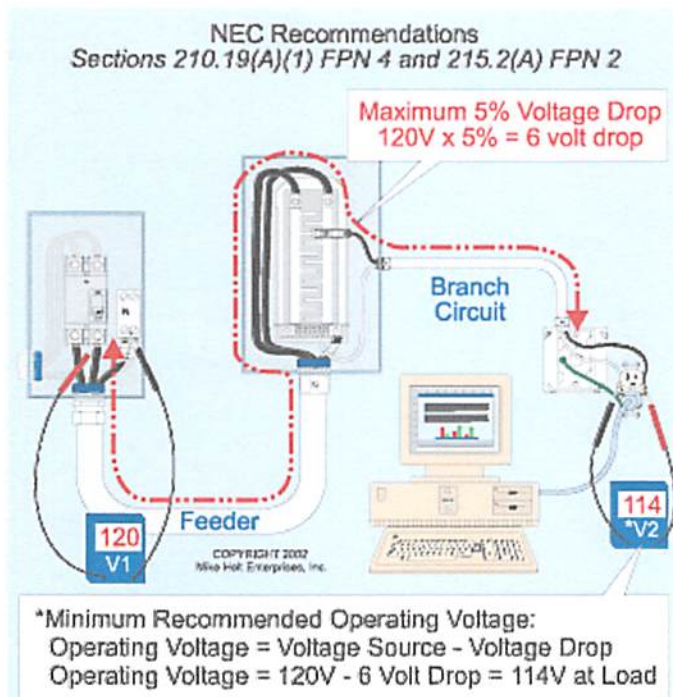


Fig. 2. The total voltage drop of the feeder and branch circuit shouldn't exceed 5% of the source.

To test your knowledge, take the following pop quiz. What is the minimum NEC-recommended operating voltage for a 115V load connected to a 120V source (Fig. 2)?

- (a) 120V
- (b) 115V
- (c) 114V
- (d) 116V

The maximum conductor voltage-drop recommended for both the feeder and branch circuit is 5% of the voltage source (120V). The total conductor voltage drop (feeder and branch circuit) shouldn't exceed $120V \times 0.05 = 6V$. Calculate the operating voltage at the load by subtracting the conductor voltage drop from the voltage source: $120V - 6V = 114V$. Therefore, the correct answer is (c), 114V.

Doing the calculations. You can determine conductor voltage drop by using the Ohm's Law method or by the formula method, but you can only use the Ohm's Law method ($I \times R$) for single-phase systems. Regardless of which method you use, observe the following:

- For conductors 1/0 AWG and smaller, the difference in resistance between DC and AC circuits is so little that it can be ignored. In addition, you can ignore the small difference in resistance between stranded and solid wires.
- VD = Voltage drop
- I = The load in amperes at 100%, not 125%, for motors or continuous loads
- R = Conductor resistance, Chapter 9, Table 8 for DC or Chapter 9, Table 9 for AC

Let's do a sample calculation using the Ohm's Law method. What is the voltage drop of two 12 AWG THHN conductors that supply a 16A, 120V load located 100 feet from the power supply?

- (a) 3.2V
- (b) 6.4V
- (c) 9.6V
- (d) 12.8V

The math is straightforward:

$$VD=I \times R$$

$$I=16A$$

$$R=2 \text{ ohms per } 1,000 \text{ feet, according to Chapter 9, Table 9: } (2 \text{ ohms} \div 1,000 \text{ ft}) \times 200 \text{ ft} = 0.4V$$

$$VD=16A \times 0.4V = 6.4V$$

Therefore, the correct answer is (b), 6.4V.

Formula method.. This method is slightly more involved than the Ohm's Law method, but the big advantage is you can use it for single-phase or 3-phase systems. Here are some additional items to observe:

- Single-phase $VD=(2 \times K \times I \times D) \div CM$.
- 3-phase $VD=(1.732 \times K \times I \times D) \div CM$.
- K=Direct-current constant. K represents the DC resistance for a 1,000-circular mils conductor that is 1,000 feet long, at an operating temperature of 75°C. K is 12.9 ohms for copper and 21.2 ohms for aluminum.
- Q=Alternating-current adjustment factor. For AC circuits with conductors 2/0 AWG and larger, you must adjust the DC resistance constant K for the effects of self-induction (eddy currents). Calculate the "Q" Adjustment Factor by dividing the AC ohms-to-neutral impedance listed in Chapter 9, Table 9 by the DC resistance listed in Chapter 9, Table 8.
- I = The load in amperes at 100% (not at 125% for motors or continuous loads)
- D = The distance between the load and the power supply. When calculating conductor distance, use this distance plus any up or down distance. An approximation is good

enough. For example, the load is 140 feet from the source, but the circuit goes up 10 feet into the ceiling, then down 10 feet from the ceiling to the load. The total distance would be 160 feet.

- CM = The circular mils of the circuit conductor as listed in NEC Chapter 9, Table 8

Let's look at a 3-phase example. A 3-phase, 36kVA load rated 208V is wired to the panelboard with 80-foot lengths of 1 AWG THHN aluminum. What is the approximate voltage drop of the feeder circuit conductors?

(a) 3.5V

(b) 7V

(c) 3%

(d) 5%

Applying the 3-phase formula, where:

$K=21.2$ ohms, aluminum

$I=[36,000 \text{ VA} \div (208\text{V} \times 1.732)]=100\text{A}$

$D=80$ ft

$CM=83,690$ (obtained from Chapter 9, Table 8)

$VD=(1.732 \times 21.2 \times 100\text{A} \times 80 \text{ ft}) \div 83,690 \text{ CM}=3.51\text{V}$

Therefore, the correct answer is (a), 3.5V.

Don't forget to verify that you haven't exceeded the recommended Code requirement of a 3% voltage drop at the end of the branch circuit or feeder.

$\%VD=(3.51\text{V} \div 208\text{V}) \times 100=1.69\%$

Algebraic variations. Using basic algebra, you can apply the same basic formula to find one of the other variables if you already know the voltage drop. For example, suppose you want to know what size conductor you need to reduce the voltage drop to the desired level. Simply rearrange the formula. For 3-phase, it would look like this:

$CM \text{ (3-phase)}=(1.732 \times K \times I \times D) \div VD$

**Conductor Sizing
"CM" Formula - 3-Phase**

D = 390 ft

Load
15 kVA
3-Phase

480
V1

Calculate the conductor size.

Formula:

$$CM = \frac{\sqrt{3} \times K \times I \times D}{\text{allowable VD}}$$

CM = ?
 $\sqrt{3} = 1.732$
 K = 12.9 ohms, copper
 I = 18A
 D = 390 ft
 VD = (480v x 0.03) = 14.4V

$CM = \frac{1.732 \times 12.9 \text{ ohms} \times 18A \times 390 \text{ ft}}{14.4 \text{ voltage drop}} = 10,892 \text{ cm}$

Chapter 9, Table 8, 10,892 cm = **8 AWG conductors**

Fig. 3. Select an appropriate size conductor to limit voltage drop on the circuit to less than 3%.

Remember, for single-phase calculations you would use 2 instead of 1.732.

Suppose you have a 3-phase, 15kVA load rated 480V and 390 feet of conductor. What size conductor will prevent the voltage drop from exceeding 3% (Fig. 3)?


K=12.9 ohms, copper

$I = [15,000 \text{ VA} \div (480V \times 1.732)] = 18A$

D=390 ft

VD=480V×0.03=14.4V

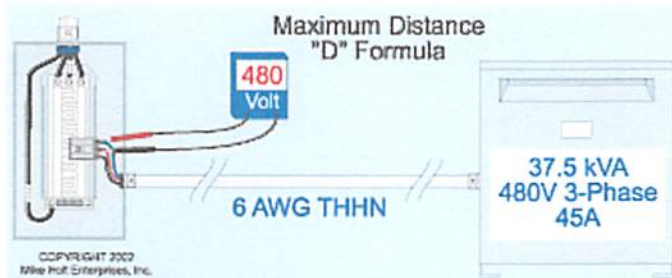$CM = (1.732 \times 12.9 \times 18A \times 390 \text{ ft}) \div 14.4V = 10,892 \text{ CM}$ (8 AWG, Chapter 9, Table 8)



Calculate distance of conductors.

Formula:

$$D = \frac{CM \times VD}{\sqrt{3} \times K \times I}$$

$D = ?$
 $CM = 26,240$
 $VD = 480V \times 0.03 = 14.4V$
 $\sqrt{3} = 1.732$
 $K = 12.9 \text{ ohms, copper}$
 $I = 45A$

$$D = \frac{26,240 \text{ cm} \times 14.4VD}{1.732 \times 12.9 \text{ ohms} \times 45A} = 376 \text{ ft}$$

Fig. 4. Calculating the maximum distance you can install a transformer from its panelboard is simple if you know the circular mils and direct-current constant of the circuit conductor, load in amperes at 100%, and assume a minimum voltage drop of 3%.

You could also rearrange the formula to solve a problem like this one: What is the maximum length of 6 AWG THHN you can use to wire a 480V, 3-phase, 37.5kVA transformer to a panelboard so voltage drop doesn't exceed 3% (Fig. 4 at left)?

$$D (3\text{-phase}) = (CM \times VD) \div (1.732 \times K \times I)$$

$$CM = 26,240 \text{ (6 AWG Chapter 9, Table 8)}$$

$$VD = 480V \times 0.03 = 14.4V$$

$$K = 12.9 \text{ ohms, copper}$$

$$I = [37,500 \text{ VA} \div (480V \times 1.732)] = 45A$$

$$D = (26,240 \text{ CM} \times 14.4V) \div (1.732 \times 12.9 \text{ ohms} \times 45A) = 376 \text{ ft}$$

Maximum Loads
"I" Formula

Power Source
460V 3-Ph

Distance = 300 ft

1 AWG THHN

Calculate the maximum load on conductor.

Formula:

$$I = \frac{CM \times VD}{\sqrt{3} \times K \times D}$$

$I = ?$
 CM = 83,690, Chapter 9, Table 8
 VD = 460V x 0.03 = 13.8V
 $\sqrt{3} = 1.732$
 K = 12.9 ohms, copper
 D = 300 ft

$$I = \frac{83,690 \text{ cm} \times 13.8\text{VD}}{1.732 \times 12.9 \text{ ohms} \times 300 \text{ ft}} = 172\text{A}$$

Check: Table 310.16, 75° C, 1 AWG THHN is limited to 130A. The maximum recommended voltage drop is not exceeded, but Table 310.16 requirements are violated.

Fig. 5. When working with existing circuits, your load will be limited by the existing conductor size and the distance from the source.

Sometimes, the only way to limit voltage drop is to limit the load. Again, you can rearrange the basic formula algebraically: $I=(CM \times VD) \div (1.732 \times K \times D)$. Suppose an installation contains 1 AWG THHN conductors, 300 feet long in an aluminum raceway fed by a 3-phase, 460/230V power source. What is the maximum load the conductors can carry without exceeding the NEC recommendation for voltage drop (Fig. 5)? Let's walk through the required calculation:

$$I=(CM \times VD) \div (1.732 \times K \times D)$$

$$CM=83,690 \text{ (1 AWG, Chapter 9, Table 8)}$$

$$VD=460\text{V} \times 0.03=13.8\text{V}$$

$$K=12.9 \text{ ohms, copper}$$

$$D=300 \text{ ft}$$

$$I=(83,690 \text{ CM} \times 13.8\text{V}) \div (1.732 \times 12.9 \text{ ohms} \times 300 \text{ ft})=172\text{A}$$

Note: The maximum load permitted on 1 AWG THHN at 75°C is 130A [110.14(C) and Table 310.16].

The NEC doesn't require you to do voltage drop calculations because they aren't involved in issues of safety, but that doesn't mean they aren't important. A system that meets NEC requirements may not be efficient in terms of power consumption or optimum in terms of equipment longevity and performance. As the old saying goes, "Wire is cheap, but performance

loss is costly.” First ensure that your system meets NEC requirements. Then look at it for voltage drop so you get the right cost tradeoffs between performance and cost

“This workforce product was funded by a grant awarded by the U.S. Department of Labor’s Employment and Training Administration. The product was created by the grantee and does not necessarily reflect the official position of the U.S. Department of Labor. The U.S. Department of Labor makes no guarantees, warranties, or assurances of any kind, express or implied, with respect to such information, including any information on linked sites and including, but not limited to, accuracy of the information or its completeness, timeliness, usefulness, adequacy, continued availability, or ownership.”



Project Product was created by North Central Missouri College Grant Staff licensed under a [Creative Commons Attribution 4.0 International License](https://creativecommons.org/licenses/by/4.0/).