

ELECTRICAL CIRCUITS

All you need to be an inventor is a good imagination and a pile of junk.

-Thomas Edison

Ohm's Law

$$I = V / R$$



Georg Simon **Ohm** (1787-1854)

I = Current (Amperes) (amps)

V = Voltage (Volts)

R = Resistance (ohms)

***How you should
be thinking about
electric circuits:***

**Voltage: a force that
pushes the current
through the circuit (in
this picture it would be
equivalent to gravity)**




***How you should
be thinking about
electric circuits:***


**Resistance: friction that
impedes flow of current
through the circuit
(rocks in the river)**



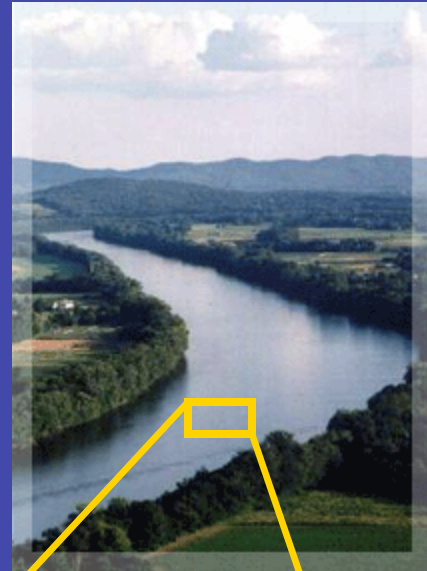***How you should
be thinking about
electric circuits:***



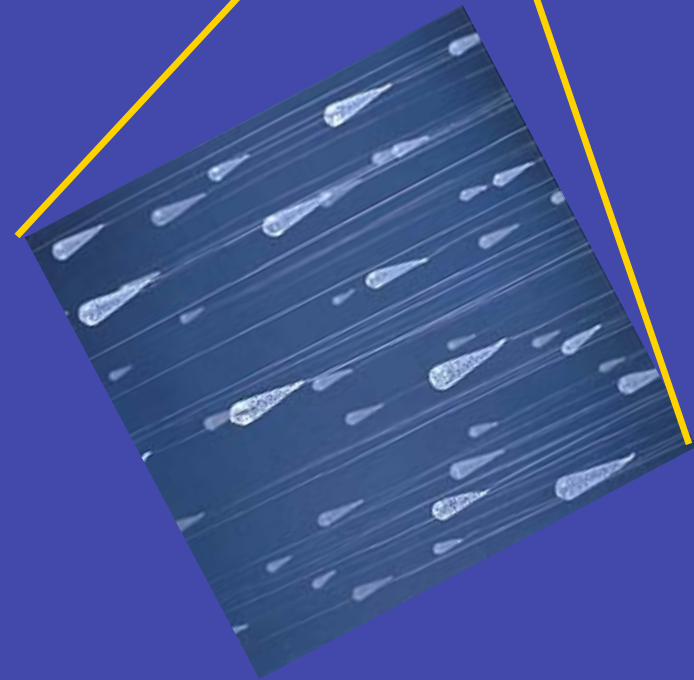**Current: the actual
“substance” that is
flowing through the
wires of the circuit
(electrons!)**



Would This Work?



Would This Work?



Would This Work?





The Central Concept: Closed Circuit



circuit diagram

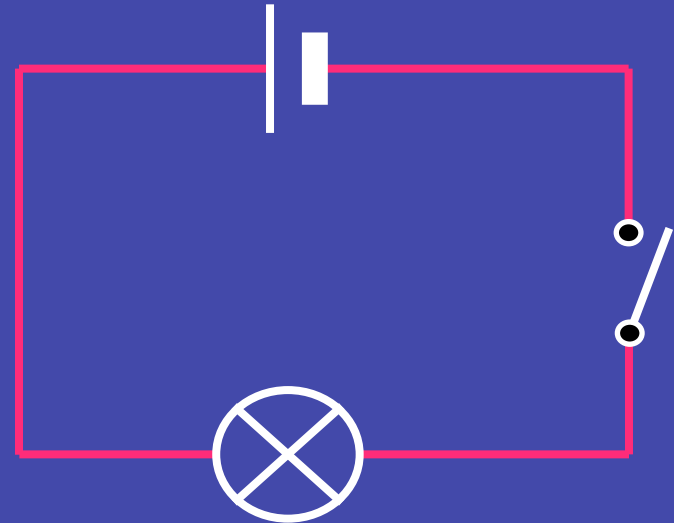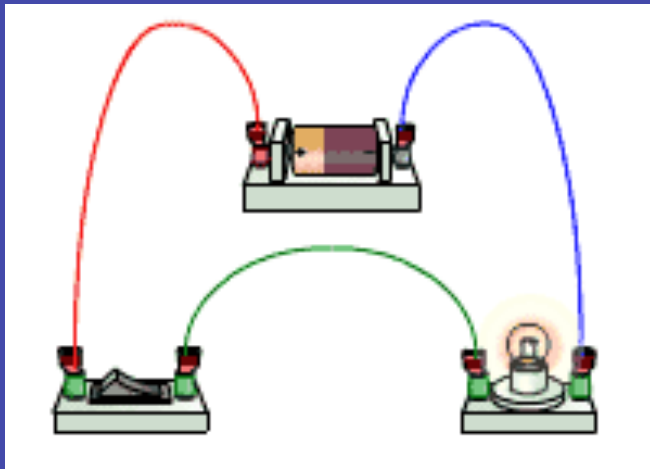Scientists usually draw electric circuits using symbols;



cell



lamp




switch




wires

Simple Circuits

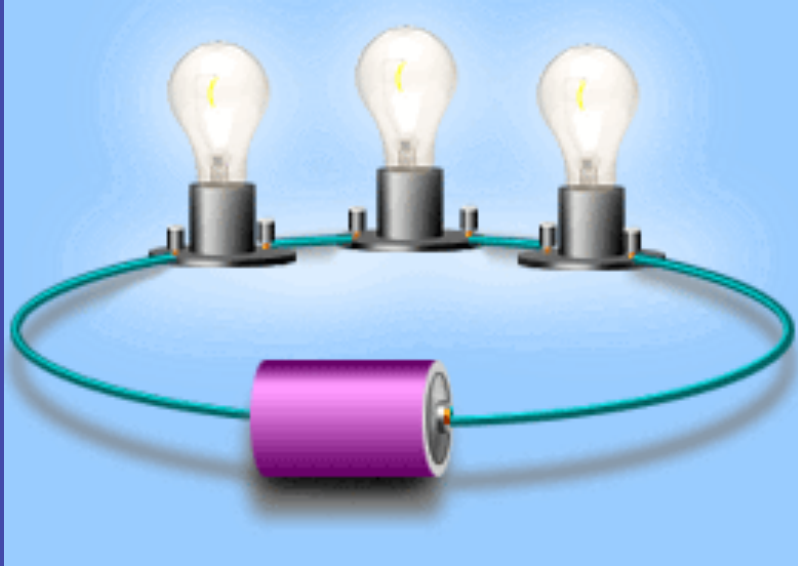

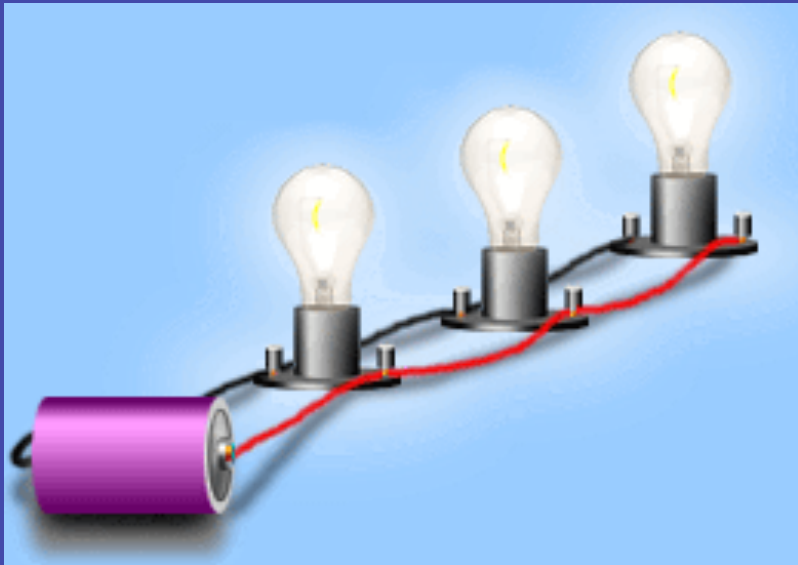- Series circuit
 - All in a row
 - **1 path** for electricity
 - 1 light goes out and the circuit is broken




- Parallel circuit
 - **Many paths** for electricity
 - 1 light goes out and the others stay on


SERIES CIRCUITS



Connect one bulb to the battery.

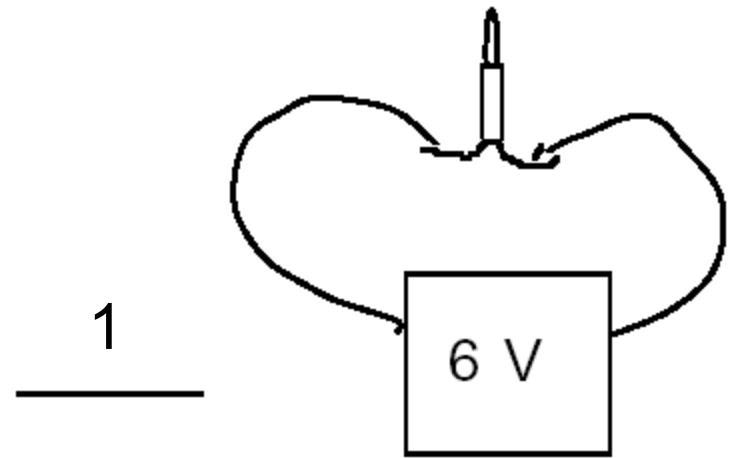

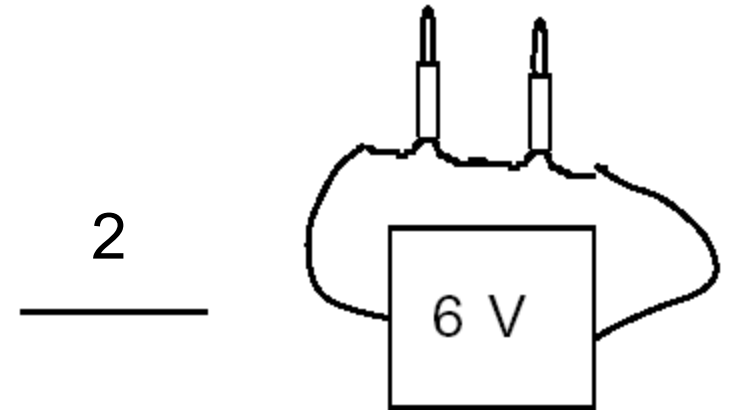Connect 2 bulbs and the battery to form a series circuit.



Connect 3 bulbs and the battery to form a series circuit.




PARALLEL CIRCUIT

- Place two bulbs in parallel. What do you notice about the brightness of the bulbs?
- Add a third light bulb in the circuit. What do you notice about the brightness of the bulbs?
- Remove the middle bulb from the circuit. What happened?


measuring current

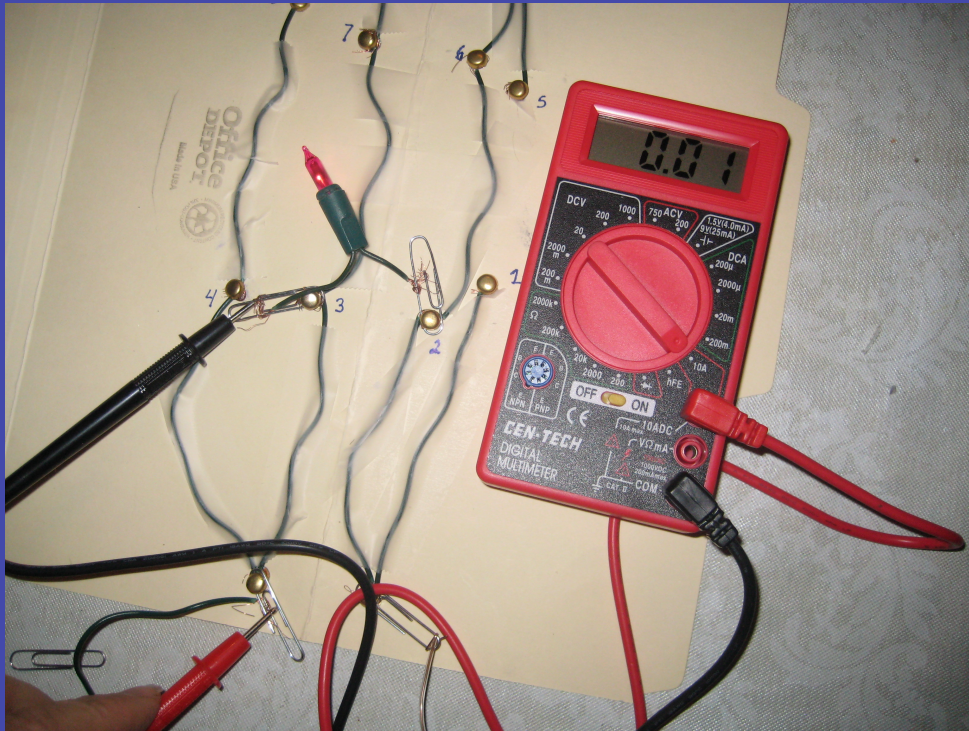Electric current is measured in **amps** (A) using an ammeter connected in series in the circuit.




measuring current

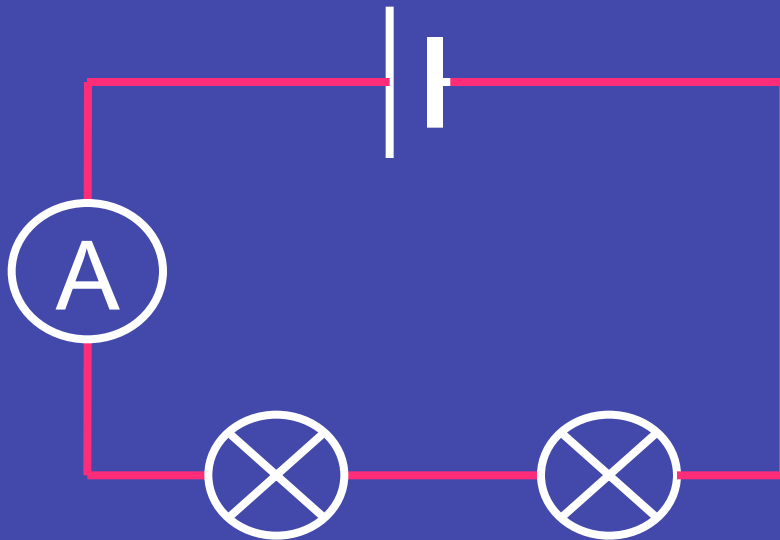This is how we draw an ammeter in a circuit.




SERIES CIRCUIT

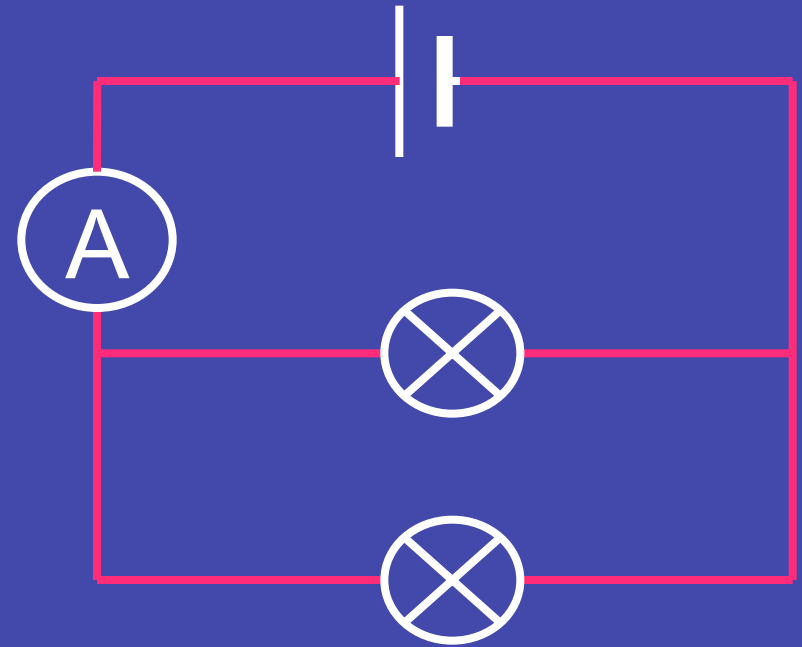

PARALLEL CIRCUIT


measuring voltage

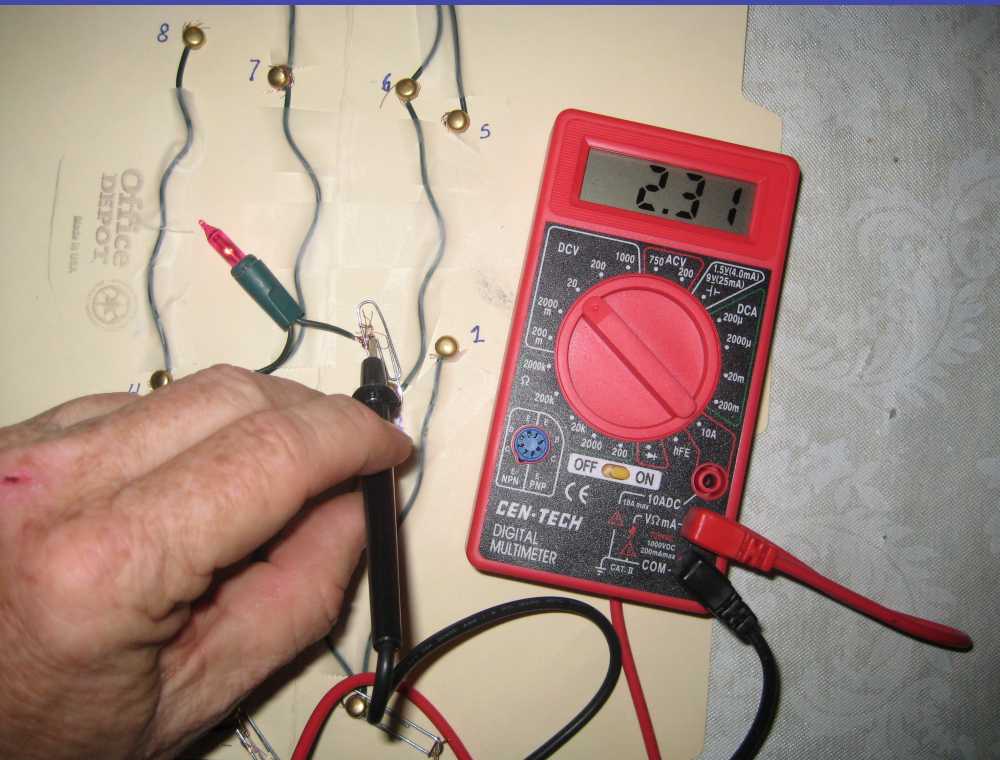The 'electrical push' which the cell gives to the current is called the voltage. It is measured in **volts (V)** on a **voltmeter**




measuring voltage

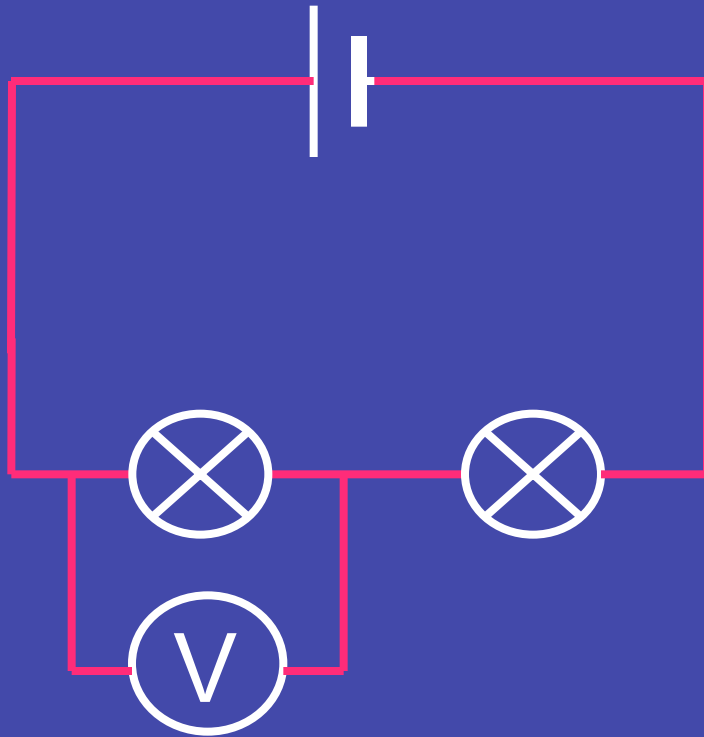This is how we draw a voltmeter in a circuit.



SERIES CIRCUIT

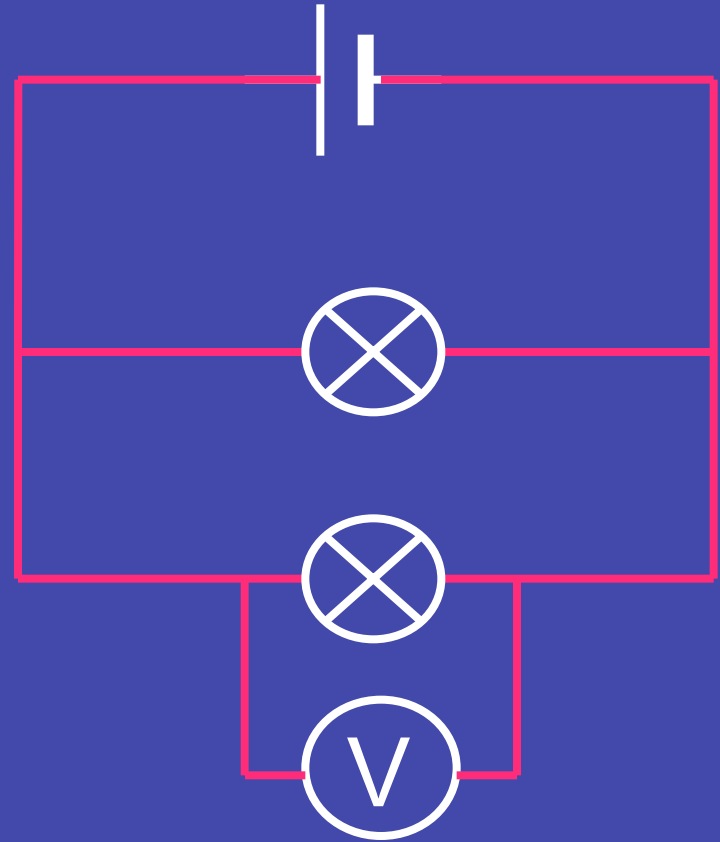

PARALLEL CIRCUIT

OHM'S LAW

- Measure the current and voltage across each circuit.
- Use Ohm's Law to compute resistance

Series Circuit

Voltage	Current	Resistance


Parallel Circuit

Voltage	Current	Resistance

measuring current


SERIES CIRCUIT

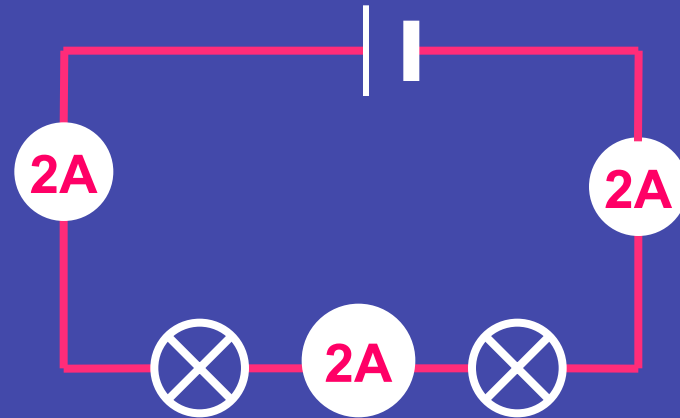- current is the **same** at all points in the circuit.





PARALLEL CIRCUIT

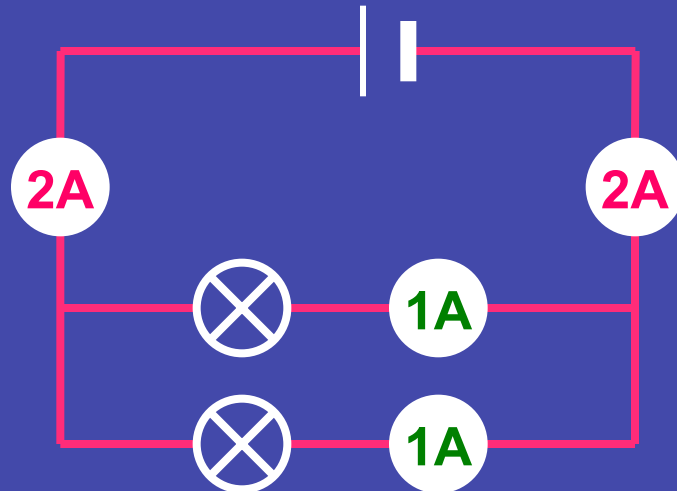- current is **shared** between the components



fill in the missing ammeter readings.

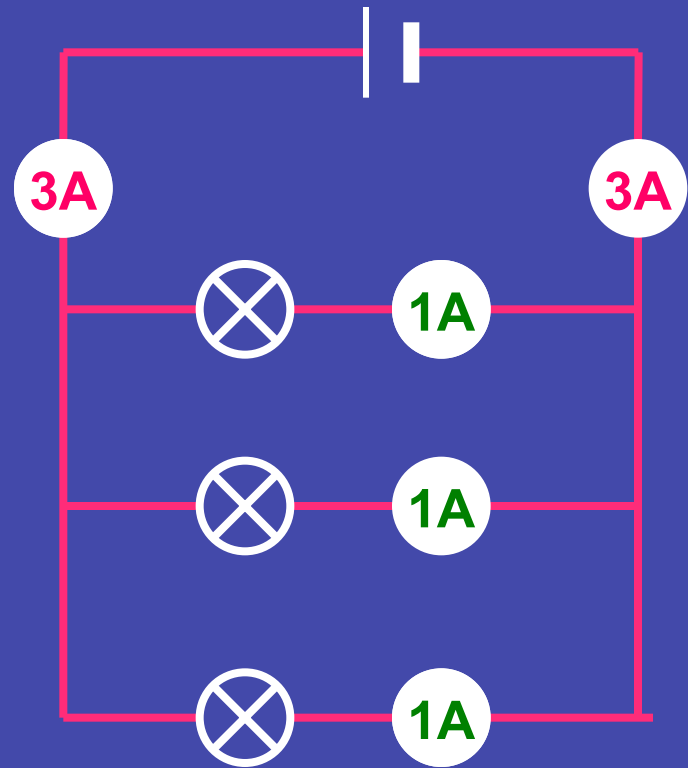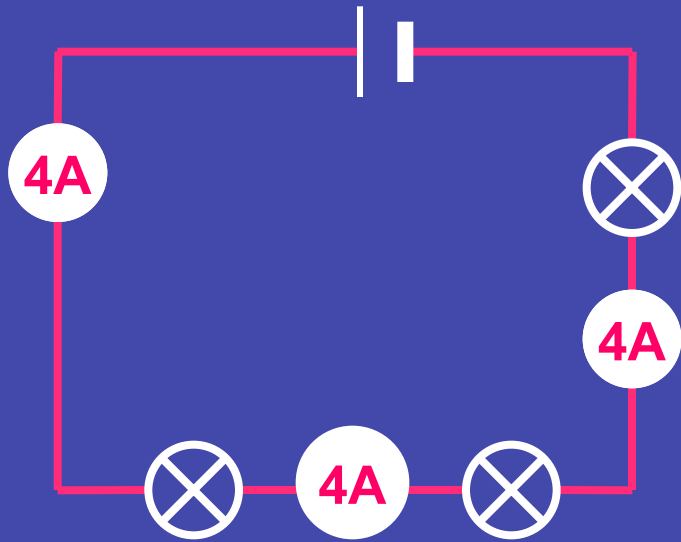

SERIES CIRCUITS

Explain what happens to the current in a series circuit when there is a break in the circuit.

The circuit is no longer complete, therefore current can not flow

Explain what happens to the voltage across each bulb as more bulbs are added to the circuit.

The voltage decreases because the current is decreased

and the resistance increases.

PARALLEL CIRCUITS

Explain what happens to the current in each bulb as more bulbs are added to the circuit.

The current remains the same. The total resistance drops in a parallel circuit as more bulbs are added

Explain what happens to the total current provided by the battery as more bulbs are added to the circuit.


The current increases.

Series and Parallel Circuits

- Series Circuits
 - only one end of each component is connected
 - e.g. Christmas tree lights


- Parallel Circuits
 - both ends of a component are connected
 - e.g. household lighting

Circuit in Diagram Form

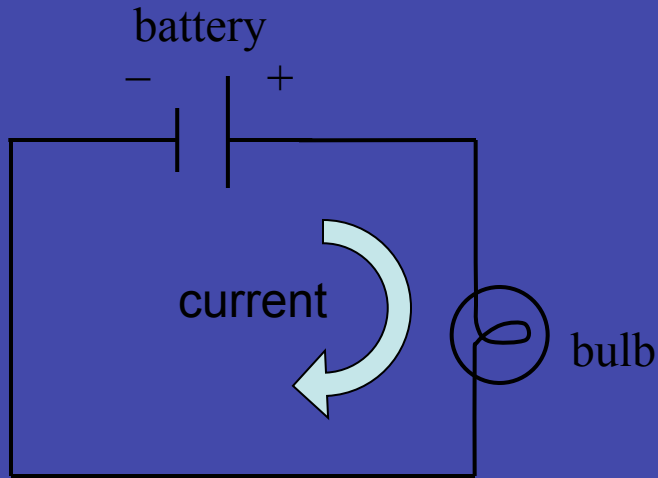

In a closed circuit, current flows *around* the loop


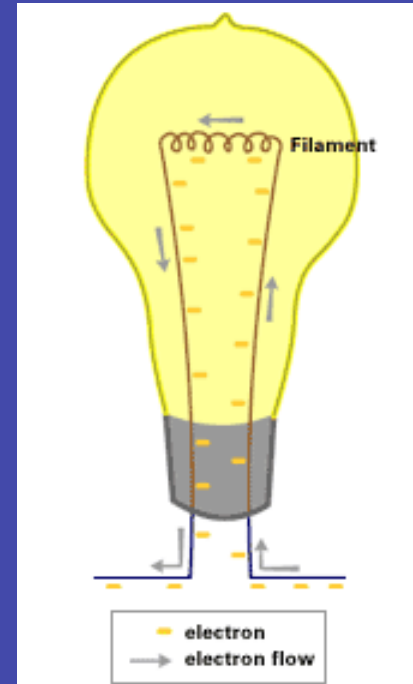
electrons flow *opposite* the indicated current direction!
(repelled by negative terminal)



Current flowing through the filament makes it glow.

No Loop → No Current → No Light

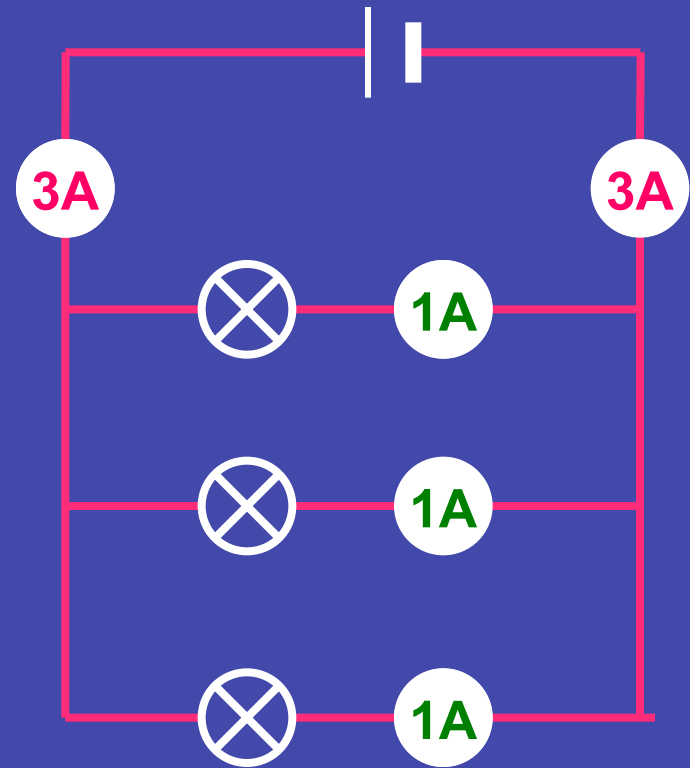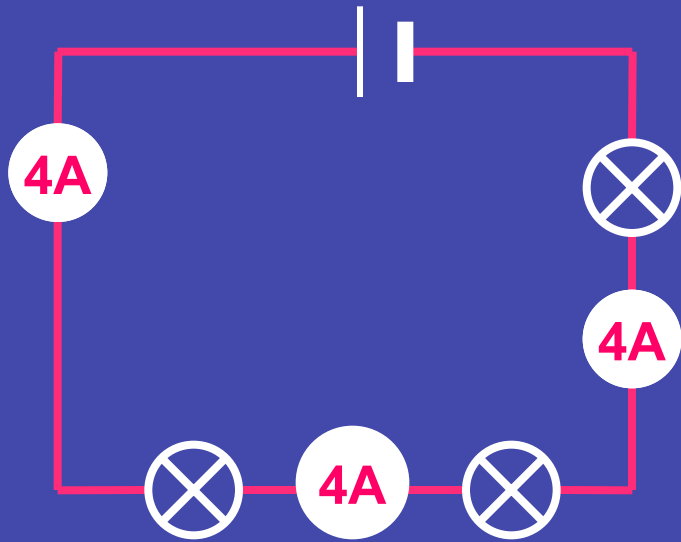copy the following circuits and fill in the missing ammeter readings.





measuring voltage

Different cells produce different voltages. The bigger the voltage supplied by the cell, the bigger the current.

Unlike an ammeter, a voltmeter is connected across the components


Scientists usually use the term **Potential Difference** (pd) when they talk about voltage.

measuring voltage

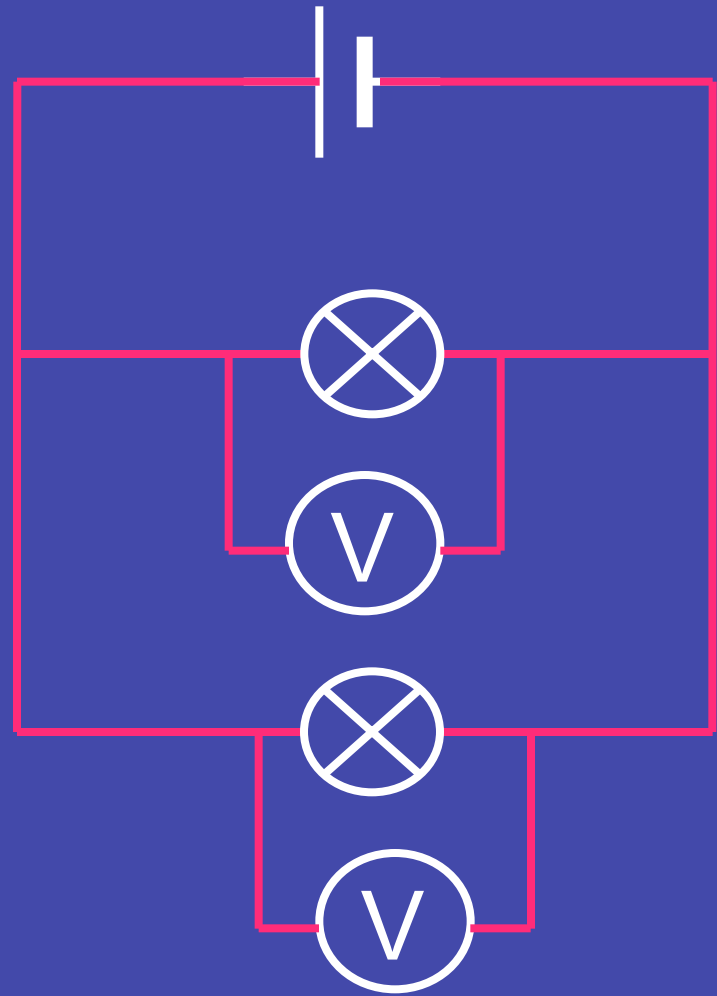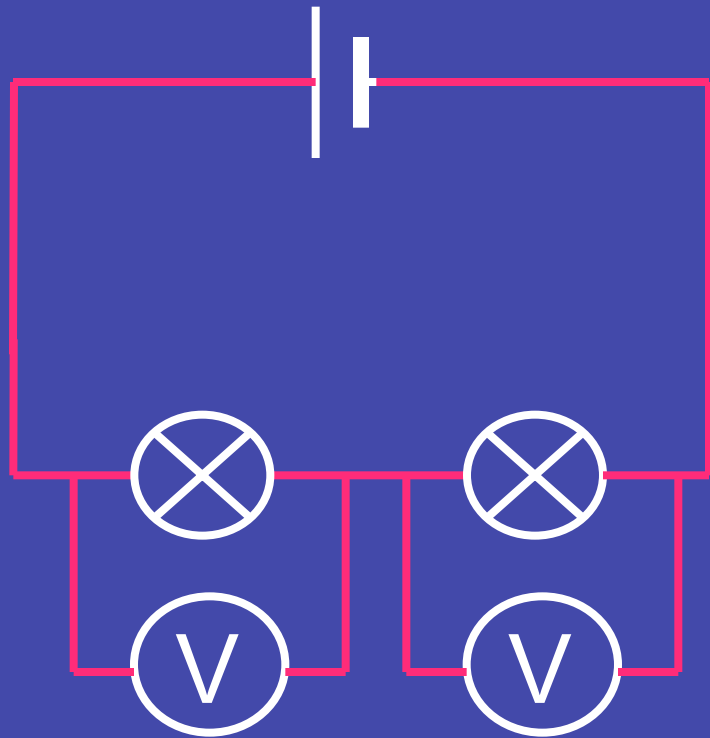


series circuit

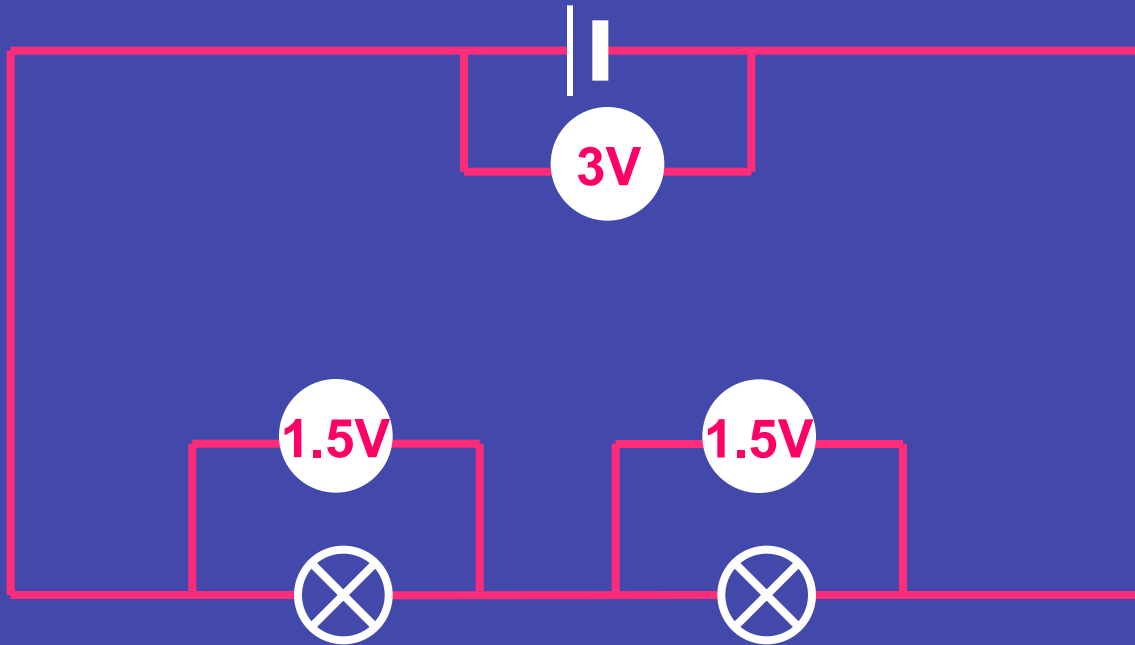- voltage is **shared** between the components



parallel circuit

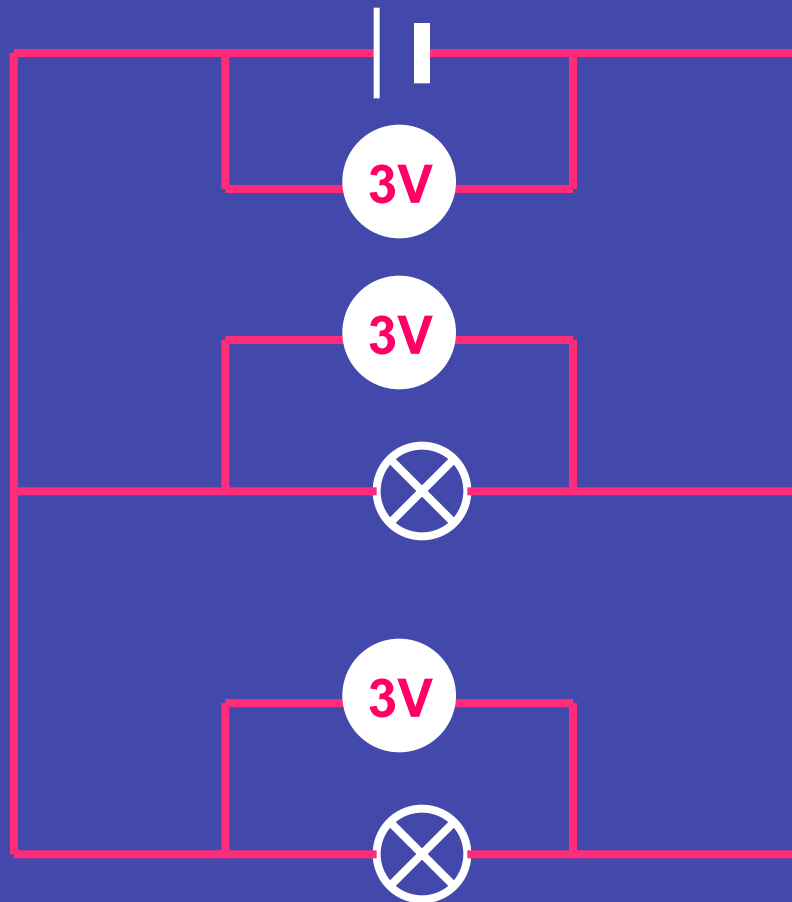- voltage is the **same** in all parts of the circuit.




measuring current & voltage

copy the following circuits on the next two slides.


complete the missing current and voltage readings.

remember the rules for current and voltage in series and parallel circuits.

measuring current & voltage

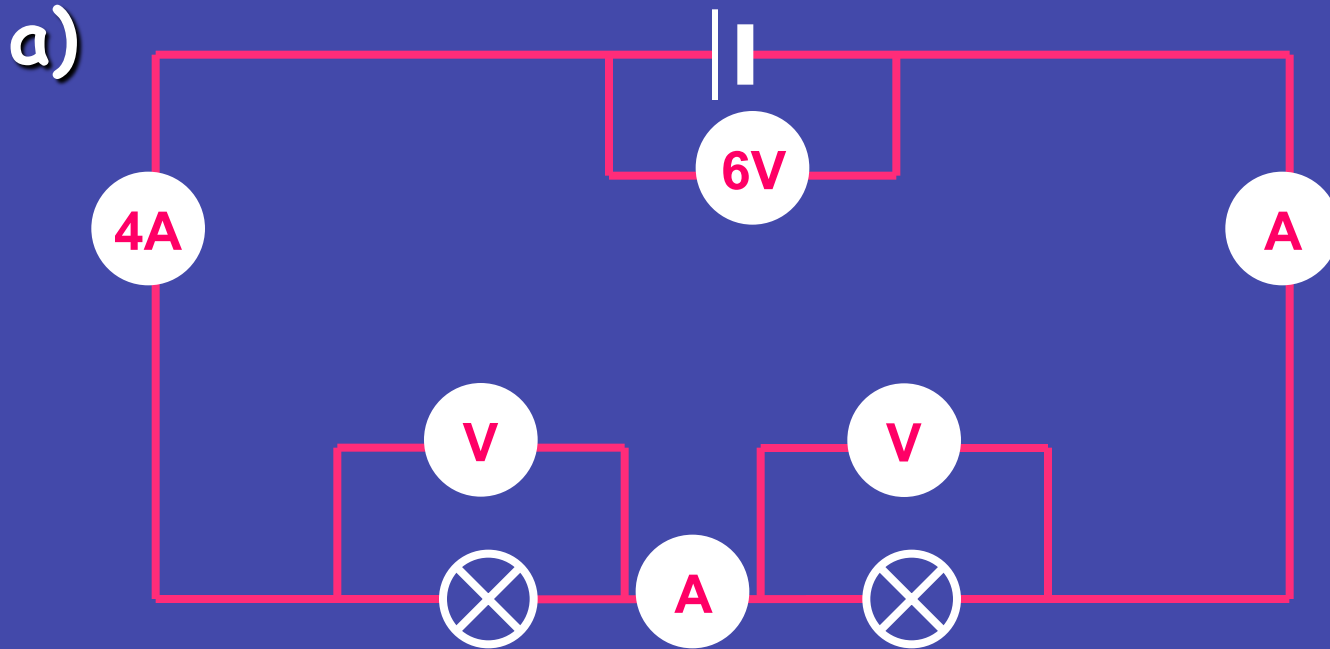


measuring current & voltage

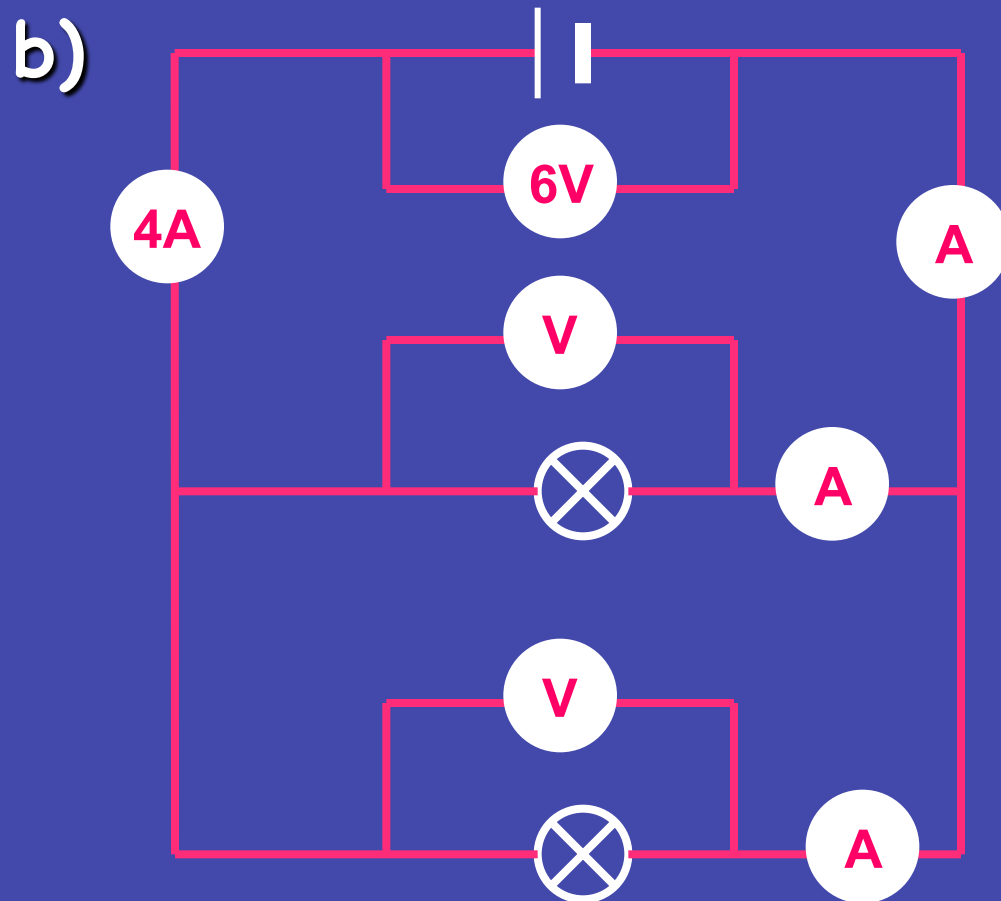


answers

a)

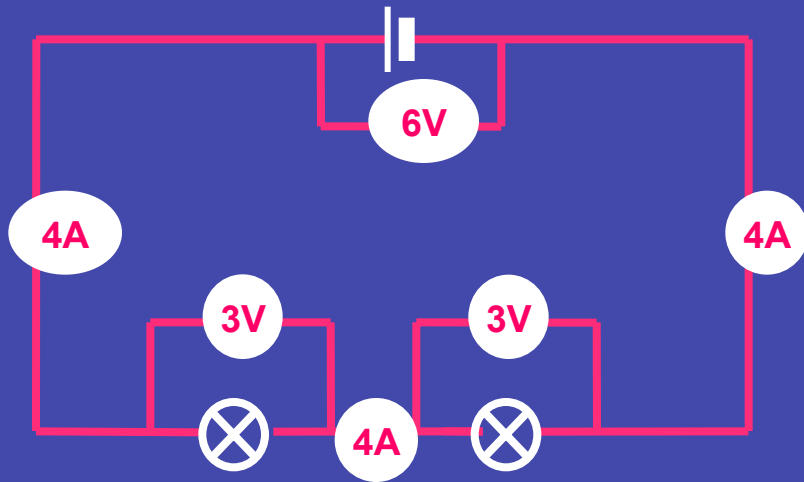

b)

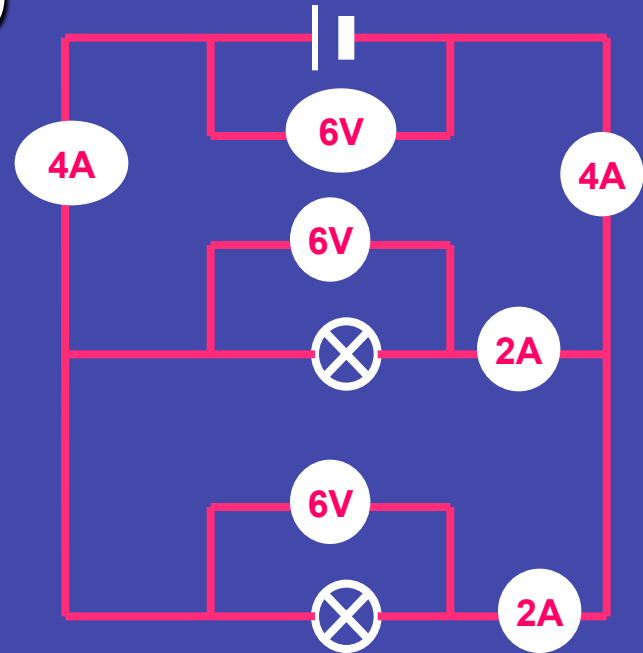

Voltage, Current, and Power

- One Volt is a Joule per Coulomb (J/C)
- One Amp of current is one Coulomb per second (6.24×10^{18} electrons/second).
- If I have one volt (J/C) and one amp (C/s), then multiplying gives Joules per second (J/s)
 - this is power: J/s = Watts
- So the formula for electrical power is just:
 $P = VI$: power = voltage \times current

“This workforce product was funded by a grant awarded by the U.S. Department of Labor’s Employment and Training Administration. The product was created by the grantee and does not necessarily reflect the official position of the U.S. Department of Labor. The U.S. Department of Labor makes no guarantees, warranties, or assurances of any kind, express or implied, with respect to such information, including any information on linked sites and including, but not limited to, accuracy of the information or its completeness, timeliness, usefulness, adequacy, continued availability, or ownership.”



Project Product was created by North Central Missouri College Grant Staff licensed under a [Creative Commons Attribution 4.0 International License](https://creativecommons.org/licenses/by/4.0/).